

Lab2 Report


Niraj Mahajan
180050069

Arithmetic Circuit

1. Implementation details

- In this question I have calculated the necessary 'conjunctions' of the input signals using AND gates
- I have used Full Adders to construct my very own Four Bit adder.
- This four bit adder is used to combine the conjunctions into our required result.

2. Diagram

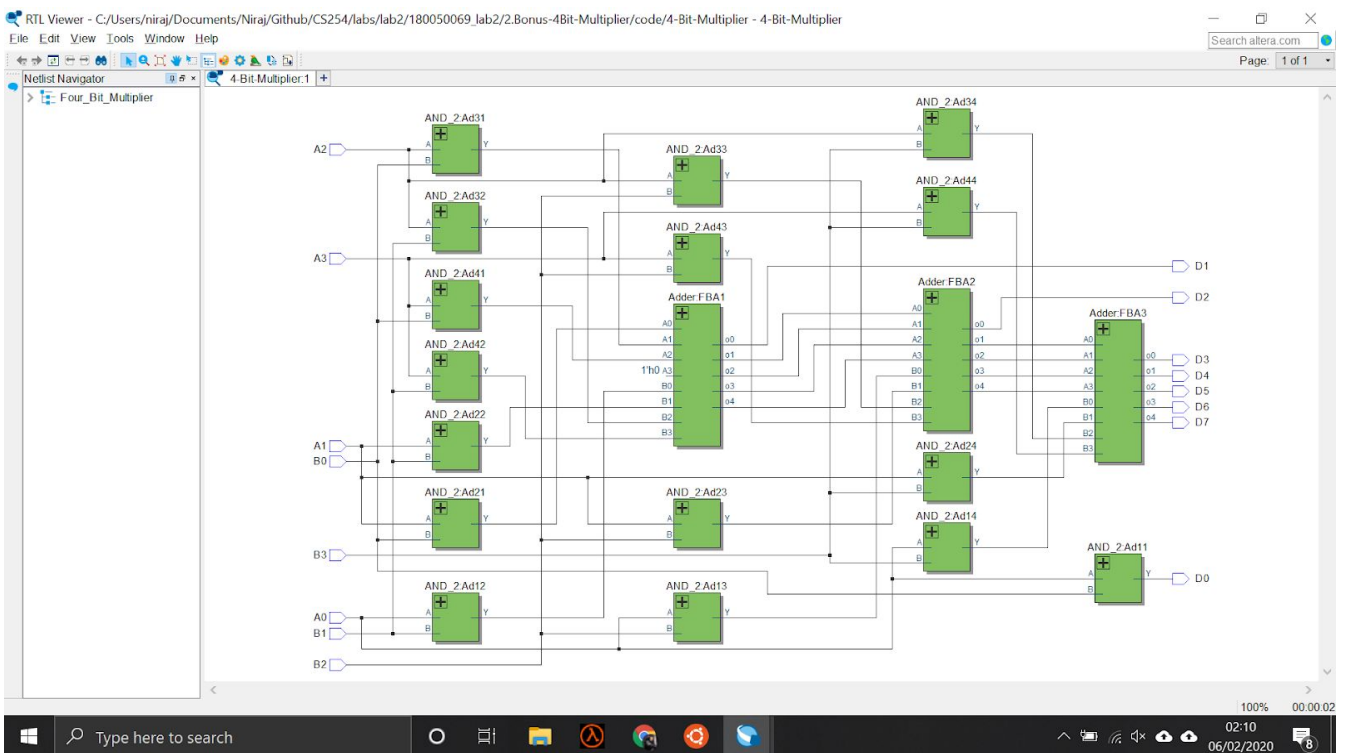

3. Simulation:

