

Niraj Mahajan
180050069

Counter

1. Implementation details
 - a. Gates used as taught in class.
 - b. If - else loop and and, xor, not & or gates used.
 - c. FSM used
2. Diagram