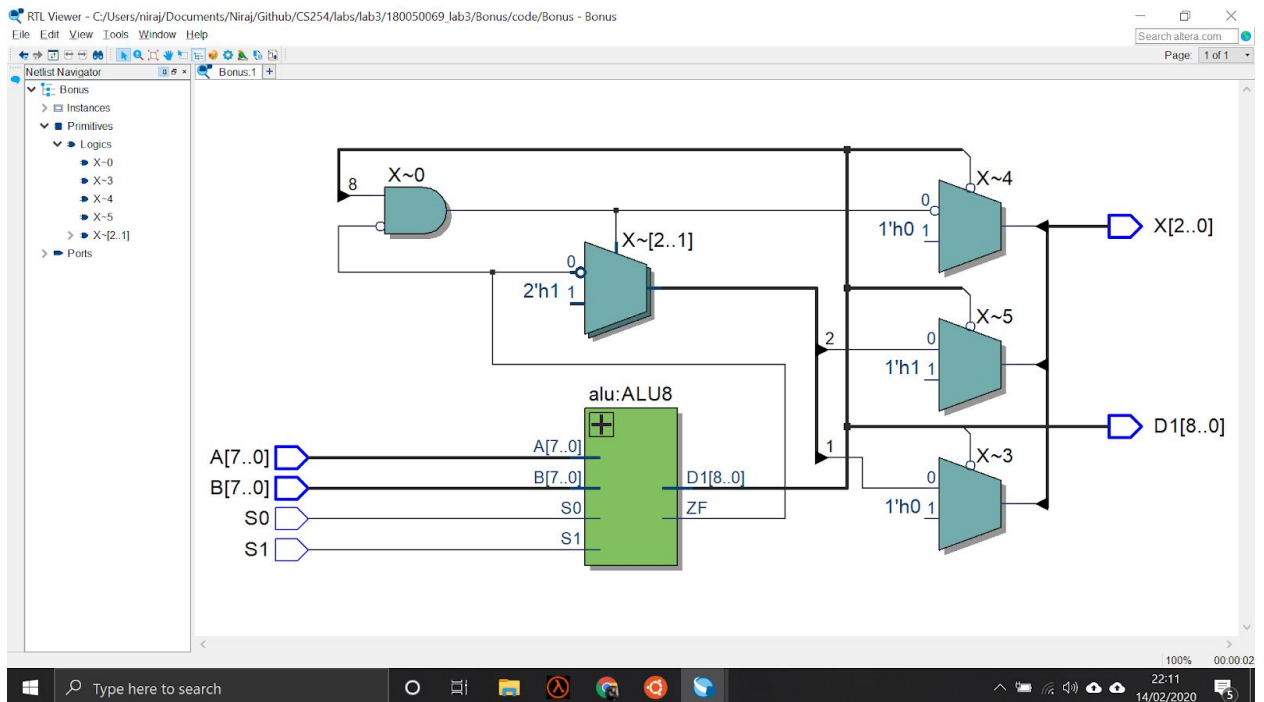


# Lab3 Report

Niraj Mahajan  
180050069

## ALU

1. Implementation details
  - a. Complete behavioral implementation.
  - b. Gates used as taught in class.
  - c. If - else loop and and, xor, not & or gates used.
2. Diagram



### 3. Simulation:

