
## **Priority Encoder**

- 1. Implementation details
  - a. Complete behavioral implementation.
  - b. Gates used as taught in class.
  - c. If else loop and and, xor, not & or gates used.

## 2. Diagram

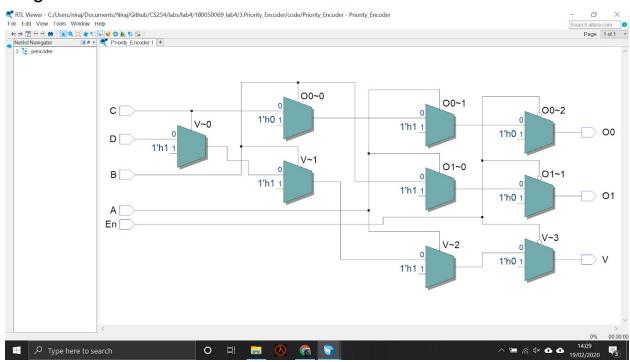

## 3. Simulation:

