


# Lab1 Report

Niraj Mahajan  
180050069

## Full Adder

Full adder using multiplexers

### 1. ROBDD :

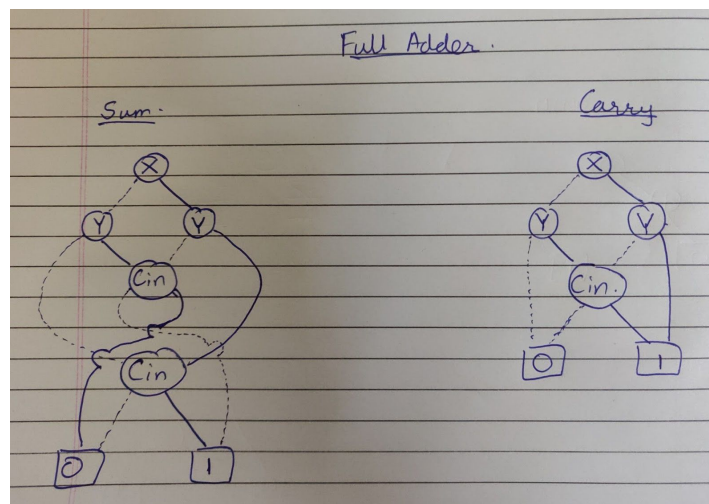

### 2. Simulation :

